
Electricity Year 4

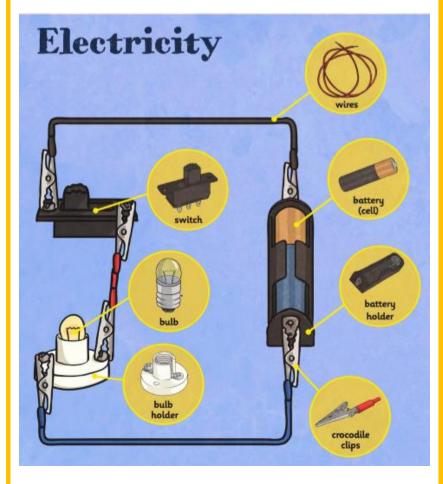

Key Questions

What appliances run on electricity?

What items are powered by battery and which are powered by mains electricity?

What components are needed to make a circuit?

Can we make a complete circuit with wires, a battery and a bulb?

What happens if we change the order of the components in a circuit?

Can circuits that are not working be fixed? How do switches work and how are they made? What is an insulator and what is a conductor?

Key Vocabulary

Appliances: A piece of equipment or device designed to perform a particular job.

Battery: A device that stores electrical energy as a chemical.

Buzzer: An electrical device that makes a buzzing sound.

Circuit: A pathway that electricity can flow around.

Conductor: A material that electricity can pass through.

Current: A flow of electricity through a wire.

Electricity: The flow of an electric current or charge through a material.

Electrons: Small particles with an electrical charge.

Generate: To make or produce.

Insulator: Any material that electricity cannot pass through.

Motor: A device that changes electrical energy into movement.

Non-renewable: This source of energy will eventually run out and so will no longer be able to be used to make electricity. These include fossil fuels - coal, oil and natural gas.

Renewable: A source of electricity that will not run out. These include solar, nuclear, geothermal, hydro and wind.

Switches: Can be open or closed. When a switch is off it 'breaks' the circuit to stop the flow of electrons.

Wire: A long thin piece of metal that carried an electrical current.